

Chapter 1 - Basic Amplifier stage

Last updated: 2 September 2003

This chapter, we look the basic tube amplifier stage. Also the theory how the amplification done.

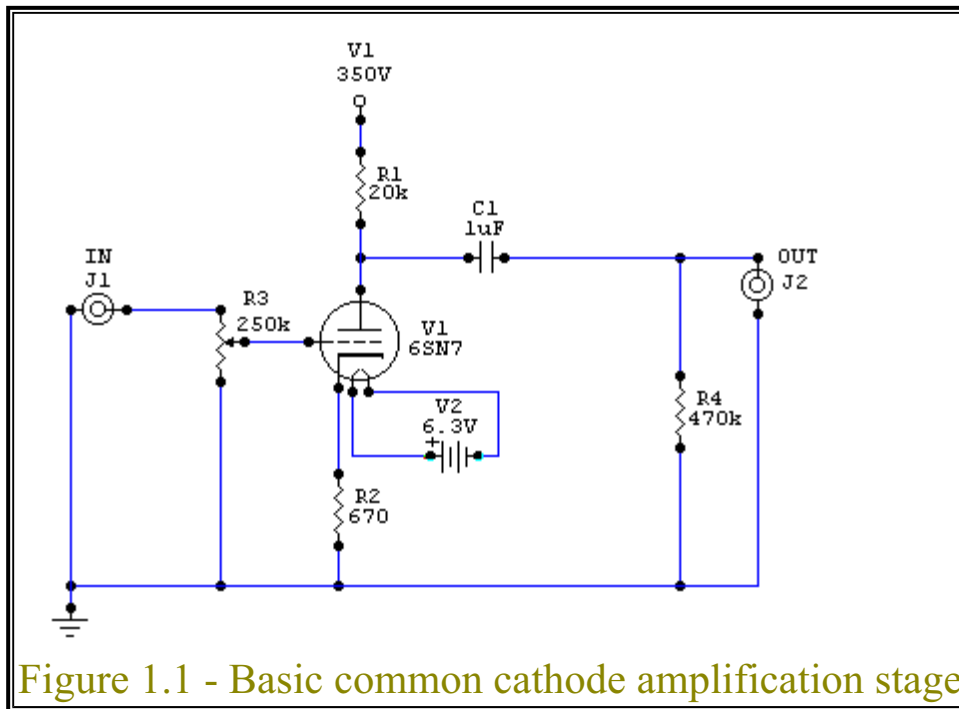


Figure 1.1 - Basic common cathode amplification stage

Basic and simple stage:

Figure 1.1 show a basic Common cathode stage. It is actually a simple voltage amplifier. Where: -

V2 is 6.3V battery supply for filament. Filament must be within + or - 5% for the tube function in the spec.

V1 is Well know call B+, it is the supply DC voltage for V1 working.

When there is a signal (AC voltage) from J1, passed throught R3 (Volume control) to adjust the sound level. The signal pass the grid of 6SN7 to the cathode and then R2 to ground.

When this circuit as a current in grid to cathode, the characteristic of the tube will allow current flow with voltage change proportional to the signal level, from Anode to cathode. The amplified signal will flow through C1 to J2.

R1 give a loading to Tube V1 6SN7, for triode It always 2 times or more the tube internal resistance

R2 control the tube working point

R3 is volume control and also the input loading to the source

R4 provide output loading

C1 is coupling capacitor which allow AC but no DC pass through

Read the Tube Menu:


Refer to General
Electronic menu:
[6SN7WGTA](#)

On the Mid-top, Three
version 6SN7 GTA,
6SN7 GTB and 12SN7
GTA are all refer to this
datasheet.

And then, "Description
and Rating" show what
this tube is and could be
used for.

Below it "General -
Electrical" show the
filament voltage, current
and AC/DC, also heater

**6SN7-GTB
6SN7-GTA
12SN7-GTA**
ET-1899
Page 1
1-54


6SN7-GTB—6SN7-GTA—12SN7-GTA
TWIN TRIODE

DESCRIPTION AND RATING

The 6SN7-GTB is a medium-mu twin triode suitable for use in a wide variety of general-purpose amplifier and phase-inverter applications. It is also especially useful as a blocking oscillator, multivibrator, or vertical-deflection amplifier in television receivers.

Electrically and physically the 6SN7-GTB is a replacement for the 6SN7-GTA. In addition, however, the 6SN7-GTB exhibits a controlled heater warm-up characteristic which makes the tube especially suited for use in television receivers which employ series-connected heaters. When the 6SN7-GTB is used in conjunction with other 600-milliamper types which have essentially the same heater warm-up characteristic, heater voltage surges across the individual tubes are minimized during the warm-up.

Except for heater and heater warm-up time ratings, the 12SN7-GTA is identical to the 6SN7-GTB.

GENERAL

Electrical	6SN7-GTA	6SN7-GTB	12SN7-GTA
Cathode—Coated Unipotential			
Heater Voltage, AC or DC	6.3	6.3	12.6 Volts
Heater Current	0.6	0.6	0.3 Amperes
Heater Warm-up Time*		10.5	... Seconds
Direct Inter-electrode Capacitances†			
	Section 1		Section 2
Grid to Plate	4.0		3.8 pF
Input	2.2		2.6 pF
Output	0.7		0.7 pF

Mechanical

Mounting Position—Any

Envelope—T-9, Glass

Base—BB-6, Intermediate Shell Octal 8-Pin
or BB-5B, Short Intermediate Shell Octal 8-Pin

BASE DIAGRAM



KEY
RTX 440

TERMINAL CONNECTIONS

Pin 1—Grid (Section 2)
Pin 2—Plate (Section 2)
Pin 3—Cathode (Section 2)
Pin 4—Grid (Section 1)
Pin 5—Plate (Section 1)
Pin 6—Cathode (Section 1)
Pin 7—Heater
Pin 8—Heater

PHYSICAL DIMENSIONS



warm-up time on the 6SN7 GTB version. Follow is the direct inter-electrode capacitance. This figure is small but very important on high frequency application. We will talk it on later chapter.

And then "General - Mechanical" show the Mounting position, tube socket and Envelope shape and material.

Refer to the right column, the bottom view of tube base shown the pin-out. Below is the name and tube size shown below.

On page 2: -

There is a "Maximum Rating"

We use 6SN7 as a Class A amp. The "Plate dissipation" 5.0W either plate and total 7.5W for both plate. We don't want the tube die fast. So, always use it with 70% the Maximum. On power tube, we sometime use up to 100%.

Another important figure is the Max plate voltage.

6SN7-GTB 6SN7-GTA 12SN7-GTA ET-1899 Page 2 10-64			
MAXIMUM RATINGS			
DESIGN-CENTER VALUES UNLESS OTHERWISE INDICATED, EACH SECTION			
	Class A Amplifier	Vertical- Deflection Amplifier ¹	
DC Plate Voltage.....	450	450 Volts	
Peak Positive Pulse Plate Voltage.....		1500 ¹ Volts	
Peak Negative Grid Voltage.....		250 Volts	
Plate Dissipation, Each Plate.....	5.0	5.0 ¹ Watts	
Total Plate Dissipation, Both Plates.....	7.5	7.5 ¹ Watts	
DC Cathode Current.....	20	20 Milliamperes	
Peak Cathode Current.....		70 Milliamperes	
Heater-Cathode Voltage			
Heater Positive with Respect to Cathode			
DC Component.....	100	100 Volts	
Total DC and Peak.....	200	200 Volts	
Heater Negative with Respect to Cathode			
Total DC and Peak.....	200	200 Volts	
Grid Circuit Resistance			
With Fixed Bias.....	1.0	. . Megohms	
With Cathode Bias.....	1.0	2.2 Megohms	
		Vertical- Oscillator Service ²	Horizontal- Oscillator Service ²
DC Plate Voltage.....	450	450 Volts	450 Volts
Peak Negative Grid Voltage.....	400	600 Volts	600 Volts
Plate Dissipation, Each Plate.....	5.0	5.0 Watts	5.0 Watts
Total Plate Dissipation, Both Plates.....	7.5	7.5 Watts	7.5 Watts
DC Cathode Current.....	20	20 Milliamperes	20 Milliamperes
Peak Cathode Current.....	70	300 Milliamperes	300 Milliamperes
Heater-Cathode Voltage			
Heater Positive with Respect to Cathode			
DC Component.....	100	100 Volts	100 Volts
Total DC and Peak.....	200	200 Volts	200 Volts
Heater Negative with Respect to Cathode			
Total DC and Peak.....	200	200 Volts	200 Volts
Grid Circuit Resistance			
With Fixed Bias.....	2.2	2.2 Megohms	2.2 Megohms
With Cathode Bias.....	2.2	2.2 Megohms	2.2 Megohms

6SN7 has a high value, but some tube could be very low. The other figure are rare to exceed, e.g. max current, heater to cathode, but we should take care.

We don't use it as Oscillator, so we look on next page.


On Page 3: -

"Characteristics and typical application" - There is 2 recommendation for Class A1 amplifier. If you are lazy to design, you can simply use that figures.

Now, just don't ask what is it. And just follow!

I will teach you how to use them on later chapter.


The the lower table:
"Class A resistance-coupled amplifier" There are many different working point for different working condition. You may choose one suitable!

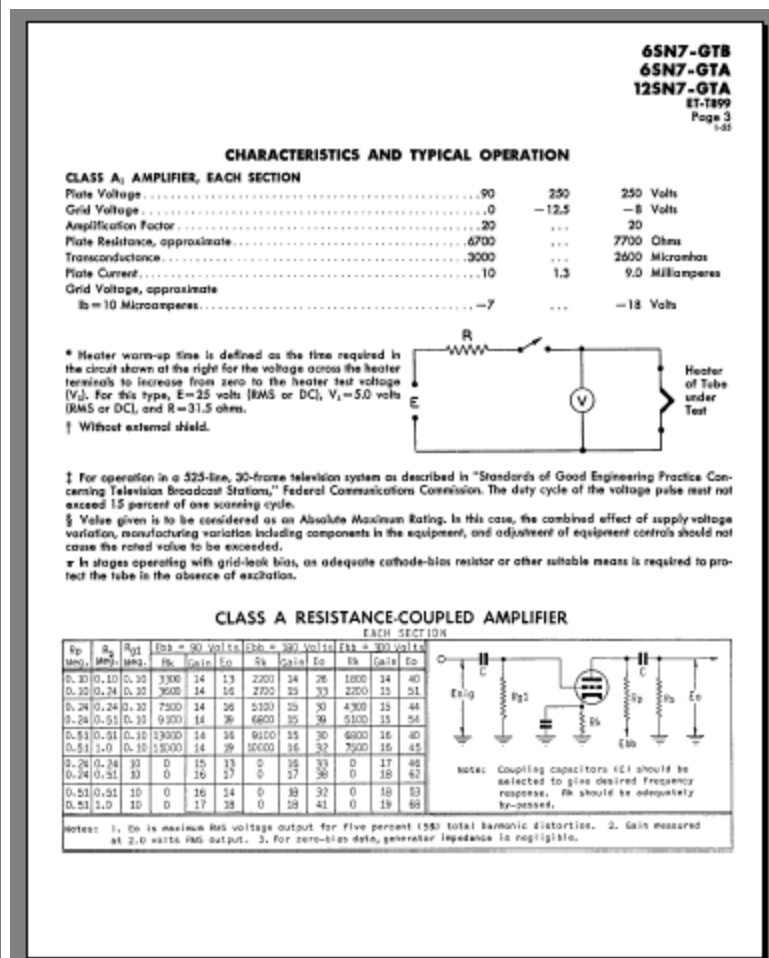

Page 4: -

There is a very important chart. Forgot the upper one.

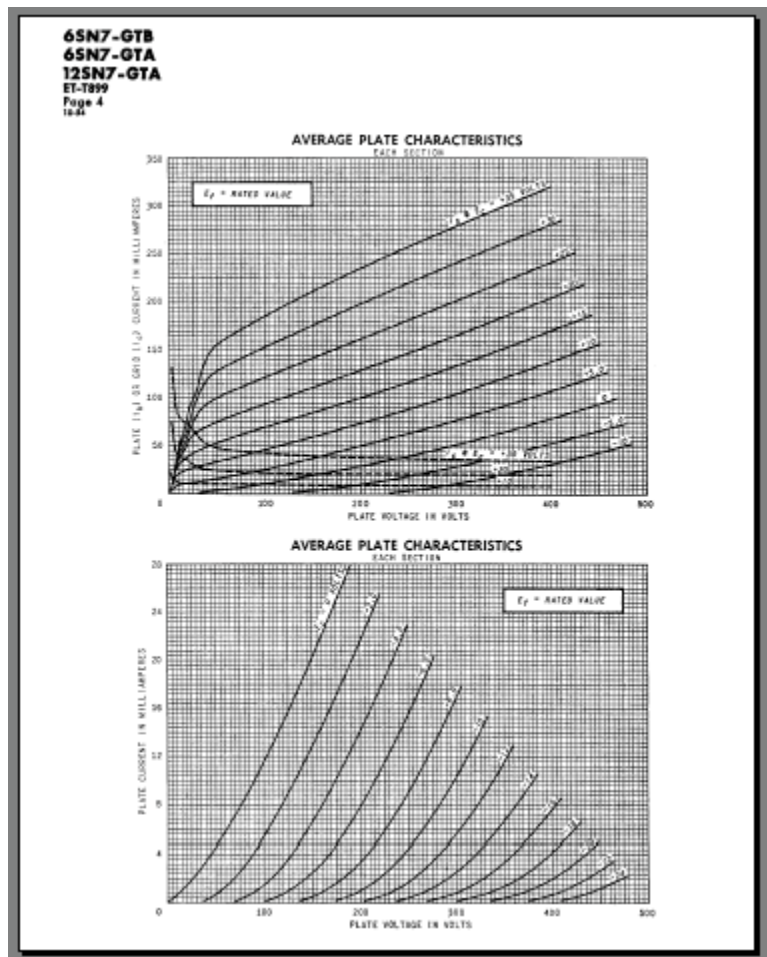The lower chart is a Class A1 amplifier chart



Design a simple "Class A resistance-coupled amplifier"

If we choose (refer to page 3 chart):-

$$B+ (E_{bb}) = 300V$$

$$R_k = 1800$$

$$\text{Gain} = 14 \text{ times}$$

as an example.

6SN7

Max Power	2.5 W
Proposed power	0.1928 W =8%
Max Plate Voltage	300 V
Plate voltage	96.4 V
Max Current	20 mA
Supply Voltage	300 V
Current	2 mA
Dropping resistor	ohm
Power	W
	300 V
Plate resistor	100000 ohm
Power	0.4 W
Plate read voltage	100 V
Proposed -BAIS	3.7 V
C. Resistor	620 ohm
Power	0.0074 W
Proposed C. resistor	1800 ohm
Voltage	3.6 V
Power	0.0072 W
Min. swing	30 V
Max. swing	160 V
AF	18.0556 times

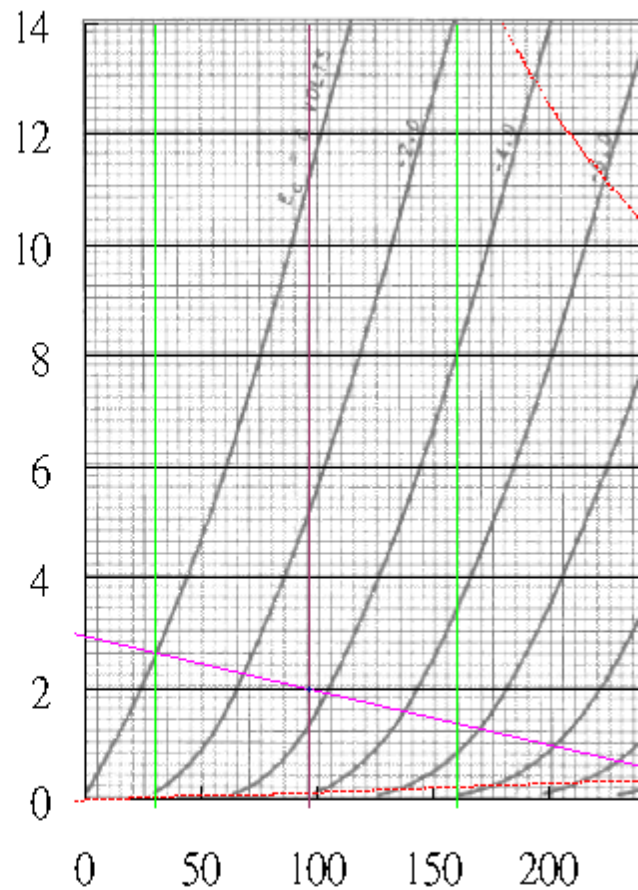


Figure 1.2 - Loading line of 6SN7

On the working point: -

if current = 0;

$$V = IR$$

$$V = 0 * 100000 = 0$$

So, the voltage is: -

$$E_{bb} - 0 = 300V$$

We draw a point on (0, 300);

if current = 2mA (0.002A),

$$V = 0.002 * 100000 = 200V$$

So, the voltage is: -

$$E_{bb} - 200V = 100V$$

We draw a point on (2, 100)

Since the $V=IR$ is a linear function, so we can join the two point (0,300) and (2,100) to get a "LOADING Line" (Purple line in Figure 1.2)

On the loading line, we choose a point which is more lower distortion. Example, the point intercept 2mA.

The voltage across R_k : -

$$V = IR = 0.002 * 1800 = 3.6V$$

On the grid line between 2 and 4, we can approx draw the point on loading line of grid = 3.6V. At there, we found the plate voltage is 96.4V

The gain is: -

$$(\Delta V_p) / (\Delta V_g)$$

$$66 / 3.6 = 18.3 \text{ times}$$

Checking: -

On Class A1, we don't allow the swing exceed zero grid.

Now we have a working point on 96.4V and 2mA: -

Maximum input swing allow = $2 * 3.6V = 7.2V$ P-P = 2.68V RMS, large enough for most sound source input

Maximum signal output/swing 130V P-P

Plate current = 2mA

Plate dissipation = $96.4V * 2mA = 0.1928 \text{ W}$ (8% of the Maximum 2.5W, safe)

So, this working point work fine

Output capacitor: -

Calculate F3: $= 1,000/(2 * \pi) / (uF * R)$)

Where: -

F3 is the frequency where -3dB roll-off

$\pi = 3.1415$

uF = Capacitance in uF

R = resistance in k ohm


In our case, say: -

0.22 uF on 100k loading

$F3 = 7.23\text{Hz}$, low enough!

Can F3 lower? Yes, just increase Rs (100k) or C1 (0.22uF). But Rs has to be match with next stage, and larger capacitor is more expensive. So, that is good enough.

Now we have a circuit: -

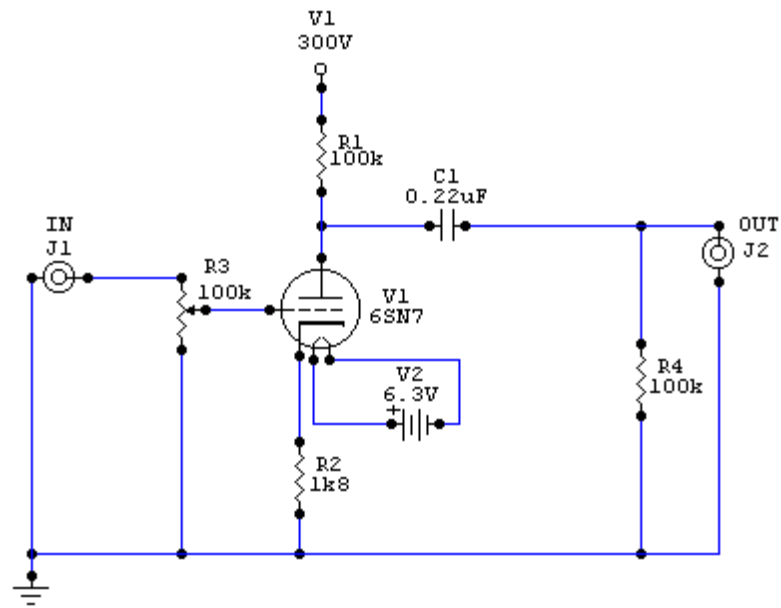

That is a simple pre-amp.