

time. When the component values are nearly optimum,  $R_1$  can have a large value, its only role being to provide a “seed” current to prime the circuit. You pay a small penalty for these advantages: The peak clamping voltage increases by several volts, because you must add the pos-

itive cycle of the resonance to the average clamping voltage and because slow diodes often exhibit a slightly poorer forward-recovery characteristic than do their fast counterparts. This characteristic results in a step of several volts at the beginning of the conduction.

Normally, these small snags should pose no problem; you can substitute the new components in a design without any other change. The circuits in **figures 1** and **2** are only two examples, but you can apply the same useful principles to a variety of other circuits. □


# Diode compensates distortion in amplifier stage

S Chekcheyev, Pridnestrovye State University, Moldova


**T**HE VOLTAGE AMPLIFIER in **Figure 1** exhibits smaller nonlinear distortion than does the conventional amplifier in **Figure 2**. Diode  $D_1$  compensates for the distortion inherent in the npn transistor. The voltage gain of a common-emitter amplifier depends on the transconductance of the transistor. The transconductance of the bipolar transistor is as follows:

$$S = \frac{eI}{k(273 + T^{\circ}C)} = nI,$$

where  $e$  is the charge of an electron,  $k$  is Boltzmann’s constant (approximately  $1.38 \times 10^{-23} \text{ J/K}$ ),  $T^{\circ}C$  is temperature in degrees Celsius,  $I$  is the emitter current, and  $n = e/[k(273 + T^{\circ}C)]$ . So, the transconductance is proportional to the emit-

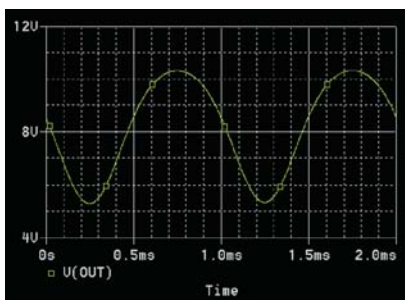


**Figure 3** Nonlinearity of the transconductance of  $Q_1$  results in this distorted waveform.

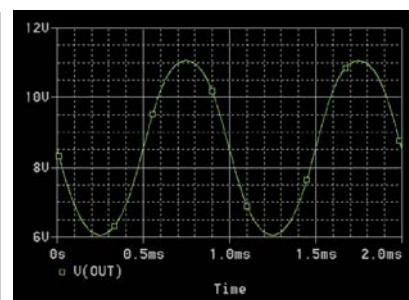


**Figure 4** The diode in the circuit of **Figure 1** produces varying, beneficial, negative feedback.

ter half-cycle (**Figure 3**).

The dynamic resistance of diode  $D_1$  in **Figure 1** is inversely proportional to the instantaneous current. That dynamic resistance forms part of the negative-feedback circuit of the amplifier. The average current of diode  $D_1$  is equal to the average emitter current of transistor  $Q_1$ . However, the instantaneous current of  $D_1$  becomes smaller, and the instantaneous dynamic resistance of  $D_1$  becomes larger when the instantaneous emitter current of  $Q_1$  becomes larger, and vice versa. Therefore, the negative feedback becomes stronger during the negative half-cycle of the output signal. As a result, the output signal of the amplifier be-

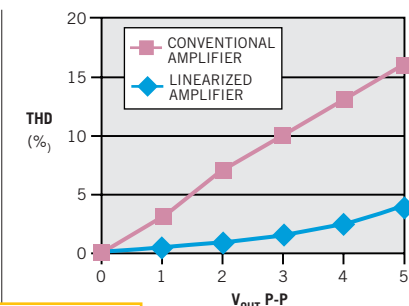


**Figure 5** The linearized amplifier produces less than one-third the harmonic distortion of the conventional amplifier.

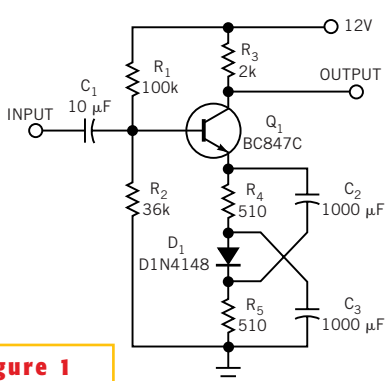

**Figure 1**

The addition of a simple diode in the emitter circuit yields the symmetric waveform of **Figure 4**.

ter current. Consequently, the instantaneous voltage-gain coefficient of the conventional common-emitter amplifier is proportional to the instantaneous emitter current. As a result, the negative half-cycle of the output signal gets more amplification than does the posi-

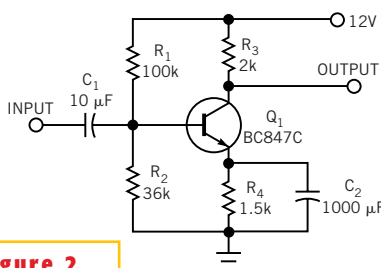

**Figure 2**

This amplifier circuit produces the distorted waveform of **Figure 3**.